

Question Bank Module 2

1. Define amplitude modulation. Explain amplitude modulation with neat waveforms
2. Derive the expression for amplitude modulated wave
3. Define modulation index for Amplitude modulated wave. Show the modulated wave for $m=1$, $m>1$ and $m<1$ where m is modulating index.
4. Derive the expression for modulation index for V_{max} and V_{min}
5. Derive the expression for total power transmitted in AM wave also the modulation index in terms of P_{total} and P_c .
6. Discuss the advantages, disadvantages and applications of AM
7. Explain diode modulator with neat circuit diagram and wave form
8. Explain transistor modulator with neat circuit diagram and waveform
9. Explain differential amplifier modulator with neat circuit diagram and waveform
10. Explain collector modulator with neat circuit diagram and waveform
11. Explain series modulator with neat circuit diagram
12. Explain diode detector with circuit diagram and waveform
13. Explain synchronous detection with circuit diagram and waveform
14. Explain balanced (Ring) modulator with neat circuit diagram and waveform
15. Define FDM. Explain FDM transmitter and receiver with neat diagram
16. EXPLAIN Telemetry transmitter and receiver with neat block diagram
17. Explain FM stereo multiplexer and recovering system with neat diagram.