

CBCS SCHEME

USN

1 S Q 2 2 E C O U 2

BEC303


**Third Semester B.E./B.Tech. Degree Supplementary Examination,
June/July 2024**

Electronic Principles and Circuits

Time: 3 hrs.


Max. Marks: 100

*Note: 1. Answer any FIVE full questions, choosing ONE full question from each module.
2. M : Marks , L: Bloom's level , C: Course outcomes.*

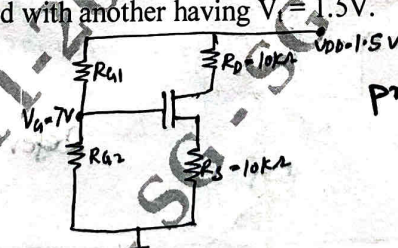Module- 1				M	L	C
Q.1	a.	Analyze voltage divider bias circuit with equations. <i>Module 1(a) page 2</i>		8	L4	CO1
	b.	Explain two supply emitter bias circuit with equations. <i>Module 1(a) page 5</i>		8	L2	CO1
	c.	If $R_1 = 10\Omega$, $R_2 = 2.2K\Omega$, $R_C = 3.6K\Omega$, $R_E = 1K\Omega$, $V_{CC} = 10V$ calculate collector to emitter voltage for voltage divider bias. <i>Refer problem page 4</i> $V_{CE} = 4.98V$		4	L3	CO1
OR						
Q.2	a.	Describe the small signal operation with diagram, write the 10 percent rule.		8	L2	CO1
	b.	Analyze common emitter amplifier with equations. <i>pages 9 & 10 any one model</i>		8	L4	CO2
	c.	Compute the output impedance for emitter follower with $R_1 = 10K\Omega$, $R_2 = 10K\Omega$, $R_E = 100\Omega$, $R_C = 100\Omega$, $V_{CC} = 30V$, $R_G = 600\Omega$, $V_{in} = 1V$. <i>Module 1(b) Refer problem page 14</i>		4	L3	CO2
Module - 2						
Q.3	a.	Explain following biasing MOS circuits: i) Fixing V_{GS} <i>page 1</i> ii) Drain to gate feedback resistor. <i>page 4</i>		8	L2	CO2
	b.	Describe small signal equivalent circuit model of MOSFET. <i>page 6</i>		6	L2	CO1
	c.	For the circuit shown in Fig.Q.3(c), determine value of V_{GS} to establish dc bias current $I_D = 0.5mA$. Device parameters are $V_t = 1V$, $K'_n W/L = 1mA/V^2$ and $X = 0$. What is percentage change in I_D when transistor is replaced with another having $V_t = 1.5V$.  <i>problem 1 page 2</i>		6	L3	CO1
		Fig.Q.3(c)				
OR						
Q.4	a.	Analyze common source amplifier without source resistance and derive expression for voltage gain. <i>page 10</i>		10	L4	CO2

	b.	Analyze common drain (source follower) amplifier and derive expression for voltage gain. pages 12 & 13	10	L4	CO2
--	----	---	----	----	-----


Module - 3

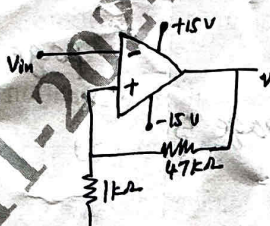Q.5	a.	Demonstrate how digital values are converted to analog values using R-2R DAC with example. pages 4 & 5	8	L3	CO4
	b.	Analyze comparator with non zero reference (positive voltage) with transfer characteristics. page 6	8	L4	CO4
	c.	If $V_{sat} = 13.5V$ computer trip points (UTP and LTP) and hysteresis for Fig.Q.5(c).  Fig.Q.5(c) $UTP = LTP = \frac{V_{sat} R_2}{R_1 + R_2}$ $= \frac{13.5(1)}{47+1}$ $= 2.36V$	4	L3	CO4

OR

Q.6	a.	Demonstrate without any input how colpitts oscillator generates output. Determine frequency of oscillations with $C_1 = 0.001\mu F$, $C_2 = 0.01\mu F$, $L = 15\mu H$. page 11, $f_0 = \frac{1}{2\pi\sqrt{LC_2}} = 1.36MHz$ $C_{eq} = C_1 C_2 = 0.999nF$	10	L3	CO2
	b.	Explain Monostable operation of 555 timer with diagram and necessary equations. page 16 & 17	10	L2	CO4


Module - 4

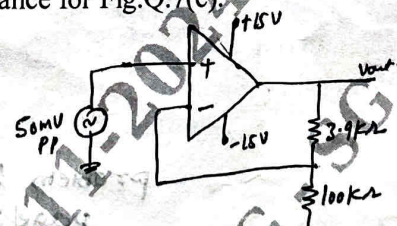Q.7	a.	Sketch four types of negative feedback topologies and explain in brief. page 2	8	L3	CO3
	b.	Analyze current controlled current source (ICIS) amplifier with equations. pages 6 & 7	6	L4	CO3
	c.	Calculate feedback fraction, closed loop voltage gain input impedance and output impedance for Fig.Q.7(c).  Fig.Q.7(c) $R_{in} = 2M\Omega$ $R_{out} = 75\Omega$ Refer problem page 4	6	L2	CO3

OR Module 4(b)

Q.8	a.	Classify filters based on ideal responses. page 2 & 3	8	L4	CO4
	b.	Explain VCVS unity gain second order low pass filter with equations. page 7 & 8	6	L2	CO4
	c.	Explain Bandstop filter with diagram and equations. page 13	6	L2	CO4

Module - 5

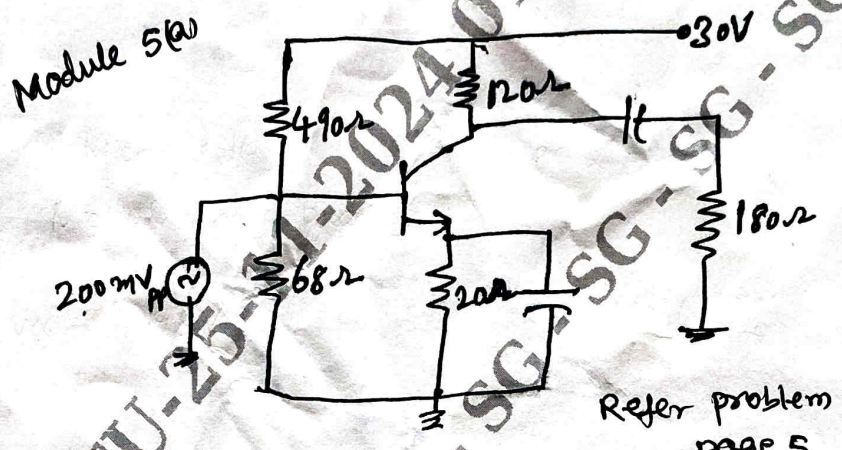Q.9	a.	Classify power amplifiers based on classes. <i>Module 5(a) page 1</i>	8	L4	CO2
	b.	What is crossover distortion? Explain operation of class B transformer coupled push pull amplifier with diagram. <i>Module 5(a) page 8 page 7</i>	8	L1	CO2
	c.	If peak to peak output voltage is 18V input impedance of base is 100Ω what is power gain for Fig.Q.9(c). <i>Module 5(a)</i>	4	L1	CO2
 Fig.Q.9(c) Refer problem page 5					
OR					
Q.10	a.	Describe structure of SCR and explain gate triggering. <i>Module 5(b) pages 2 & 3</i>	6	L2	CO5
	b.	Explain how RC circuit control SCR phase angle with circuit diagram and necessary equations. <i>pages 3 & 4 Module 5(b)</i>	8	L2	CO5
	c.	Describe UJT relation oscillator. <i>Module 5(b) page 7</i>	6	L2	CO5