

Module 3, Transient Behavior and Initial Conditions

Transient Behavior Initial Cond
Networks Can be represented using integro-differential equation. The general soln of differential equation consists of complementary function & particular integral. Complementary function represents transient response. Particular soln represents steady state response.

* n^{th} order complementary fn in differential equation consists of ' n ' no of constants. To evaluate these constants ' n ' number of initial conditions are required.

Initial Condⁿ: Initial Condⁿ of the N/w or element are the Condⁿ of the N/w (voltage, current) at the time of closing the switch at $t=0$. $t=0$ is taken as reference.


* Immediately before switching operation, these quantities are referred $v(0^-)$, $i(0^-)$, $q(0^-)$. Immediately after switching operation these quantities are referred to as $v(0^+)$, $i(0^+)$, $q(0^+)$. Why do we need I.C's:

1. They are necessary to evaluate constants during soln of a differential equation.
2. The knowledge of the initial values of one or more derivatives of a response, are helpful in anticipating the form of response.
3. Useful in understanding the behaviour of the element individually & in a network.

Initial Conditions in elements: / July 2009 (84)

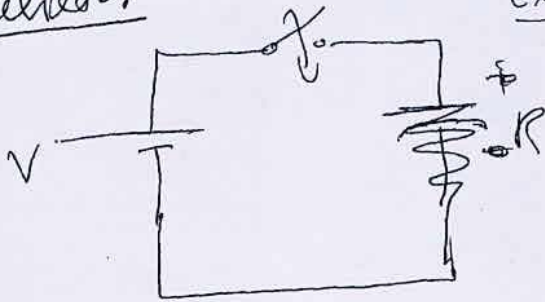
(i) Resistor

Explain transient behavior of ideal behavior of R, resistor cannot store energy



$$\therefore i_R = \frac{V}{R}$$

(ii) Inductor

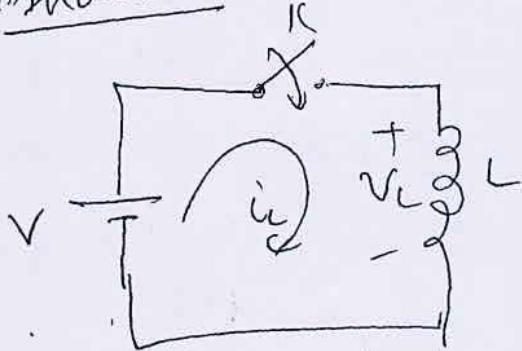

Voltage across inductor

is given by $V_L = L \frac{di_L}{dt}$

When D.C. is applied $\frac{di_L}{dt} = 0$.

$\therefore$ Under steady state Inductor acts as short ckt.
 $\therefore$ voltage across it is 0

$$i_L = \frac{1}{L} \int_{-\infty}^t V_L dt = \frac{1}{L} \int_{-\infty}^{0^-} V_L dt + \frac{1}{L} \int_{0^-}^t V_L dt$$

first term in the RHS indicates initial value of current through inductor. before closing the switch. i.e. $i_L(0^-)$

when switch is closed.


$$i_L(0^+) = i_L(0^-) + \frac{1}{L} \int_{0^-}^{0^+} V_L dt.$$

switching operation does not consume any time

$$\therefore \boxed{i_L(0^+) = i_L(0^-)}$$

ie at $t=0^+$, the inductor acts as open as the current does not change instantaneously. If initial current is present in the ~~resistor~~ ~~inductor~~ inductor, immediately after closing the switch at $t=0^+$ it acts as voltage source.

(iii) Capacitor

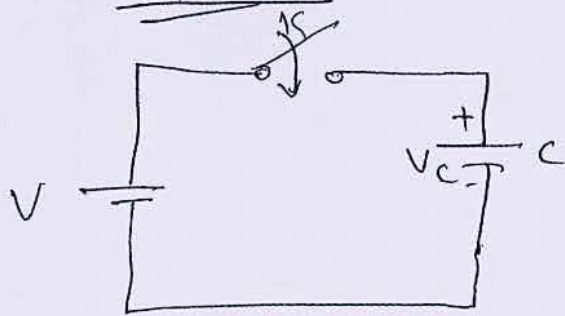

The current through the capacitance is given

$$i_c = C \cdot \frac{dv_c}{dt}$$

If a D.C. voltage is applied, $\frac{dv_c}{dt} = 0$, $i_c = 0$, Thus for D.C. quantities capacitance acts as open circuit.

Voltage across the capacitance is given by

$$V_c = \frac{1}{C} \int_{-\infty}^t i_c dt = \frac{1}{C} \int_{-\infty}^{0^-} i_c dt + \frac{1}{C} \int_{0^-}^t i_c dt$$

$$\frac{1}{C} \int_{-\infty}^{0^-} i_c dt = V_c(0^-) \text{ which is constant.}$$

When the switch 'K' is closed at $t=0$.

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i_c dt = V_c(0^-) + 0$$

$$\text{i.e. } \boxed{V_c(0^+) = V_c(0^-)}$$


i.e. Voltage across Capacitor cannot change instantaneously. Hence Capacitor does not have

any charges ~~before~~ $t=0^-$, then at $t=0^+$ its voltage will be '0'. Capacitor acts short circuit at $t=0^+$ if it does not have initial charge at $t=0^-$.


If Capacitor has initial voltage ' V_0 ', then at $t=0^+$ it acts as voltage source.

Initial Conditions

conds of elements
at $t=0^-$

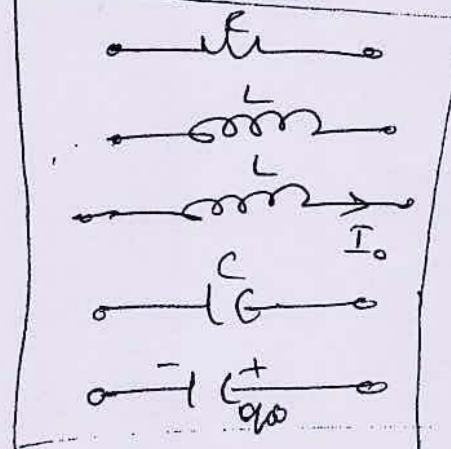


conds of elements
at $t=0^+$

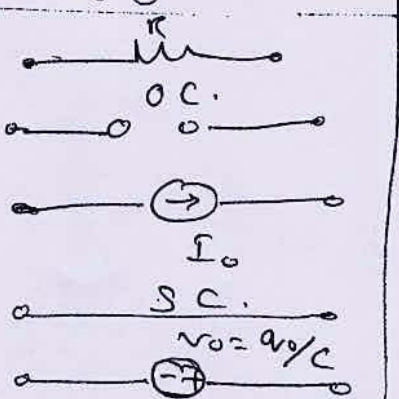


Steady state

Final Conds

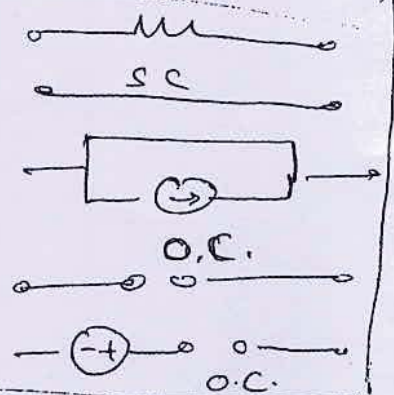

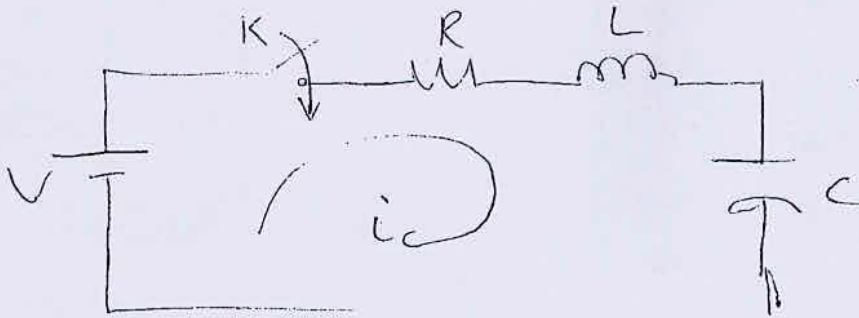Problems on Transient behavior + Initial condn (1)


- ① In the circuit shown in fig $V=10V$, $R=10\Omega$, $L=1$
 $C=10\mu F$ & $V_C(0^+)=0$, find $i(0^+)$, $\frac{di}{dt}(0^+)$ & $\frac{d^2i}{dt^2}(0^+)$



When 'K' is closed at $t=0$

$$V = Ri + L \cdot \frac{di}{dt} + \frac{1}{C} \int i dt \quad \text{--- (1)}$$

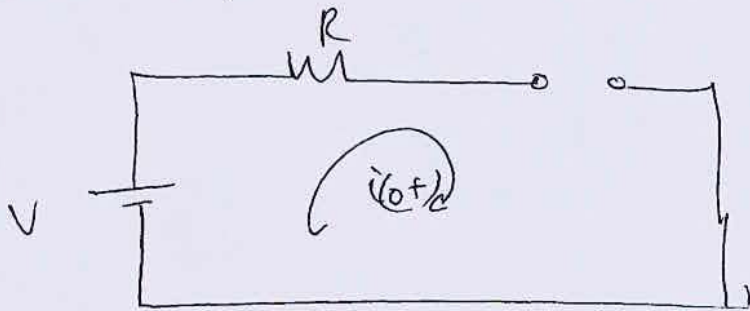at $t=0^+$, the network is as shown in fig.



Capacitor open

Inductor short

$$\boxed{i(0^+) = 0} \quad (2)$$

Sub (2) in (1)

$$V = Ri(0^+) + L \cdot \frac{di}{dt}(0^+) + \underbrace{\frac{1}{C} \int i(0^+) dt}_{V_C(0^+)}$$

given $V_C(t=0) = 0$

$$\therefore V = R \overset{10}{i(0^+)} + L \cdot \frac{di}{dt}(0^+)$$

from (2)

$$\therefore \boxed{\frac{di}{dt}(0^+) = \frac{V}{L} = \frac{10}{1} = 10 \text{ A/sec}}$$

Diff equ (1)

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

at $t = 0^+$

$$R \frac{di}{dt}(0^+) + L \frac{d^2 i}{dt^2}(0^+) + \frac{i(0^+)}{C} = 0$$


$$\therefore L \frac{d^2 i}{dt^2}(0^+) = -R \frac{di}{dt}(0^+)$$

$$\therefore \frac{d^2 i}{dt^2}(0^+) = -\frac{R}{L} \frac{di}{dt}(0^+)$$


$$= -\frac{10}{1} 10$$

$$\boxed{\frac{d^2 i}{dt^2}(0^+) = -100 \text{ A/sec}^2}$$

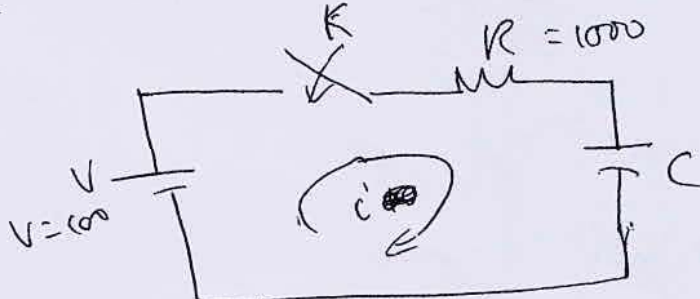(2) In the network shown in fig. the switch 'K' is closed at $t=0$, with the capacitor uncharged. Find the values of i , $\frac{di}{dt}$, $\frac{d^2 i}{dt^2}$, at $t=0^+$, for element values as follows, $V=100\text{V}$, $R=1000\Omega$, $C=1\mu\text{F}$



at $t=0^+$
eqn circuit
is as follows

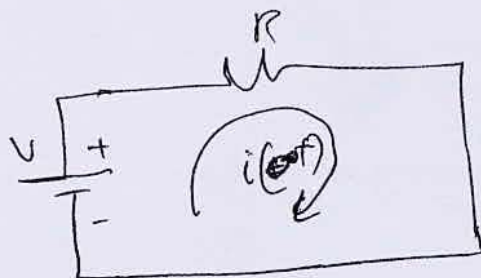

$$i(0^+) = \frac{100}{1000}$$

$$\boxed{i(0^+) = 0.1 \text{ A}}$$

- (1)

when K is closed at $t=0$.

$$V = Ri + \frac{1}{C} \int i dt$$

on differentiation $0 = R \frac{di}{dt} + \frac{i}{C} \quad \text{--- (2)}$

at $t=0+$

$$0 = R \frac{di(0+)}{dt} + \frac{i(0+)}{C}$$

$$\frac{di}{dt}(0+) = -\frac{i(0+)}{C} \cdot \frac{1}{R} = -\frac{0.1}{1 \times 10^{-6} \times 1000}$$

$$\boxed{\frac{di}{dt}(0+) = -0.1 \text{ A/sec}} \quad \boxed{-100 \text{ A/sec}}$$

Diff (2) $R \frac{d^2i}{dt^2} + \frac{1}{C} \frac{di}{dt} = 0$


at $t=0+$

$$R \cdot \frac{d^2i}{dt^2}(0+) = -\frac{1}{C} \frac{di}{dt}(0+)$$

$$\frac{d^2i}{dt^2}(0+) = -\frac{1}{RC} \frac{di}{dt}(0+) = \frac{1}{1000 \times 10^{-6}} \cdot (-100)$$

$$\boxed{\frac{d^2i}{dt^2}(0+) = 1 \times 10^6 \text{ A/m}^2}$$

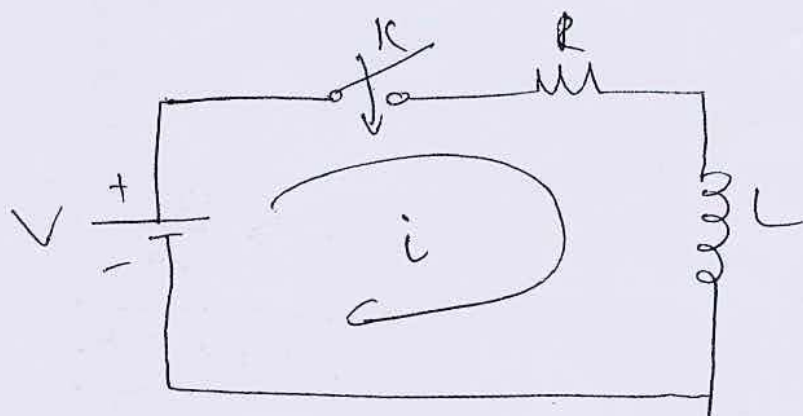
3) In the network shown in fig., K is closed at $t=0$ with zero current in the inductor. Find ' i ', $\frac{di}{dt}$, and $\frac{d^2i}{dt^2}$ at $t=0+$, if $R=10\Omega$, $L=1\text{H}$ and $V=100$



when ' K ' is closed at $t=0$

$$V = Ri + L \frac{di}{dt} \quad \text{--- (1)}$$

at $t=0+$

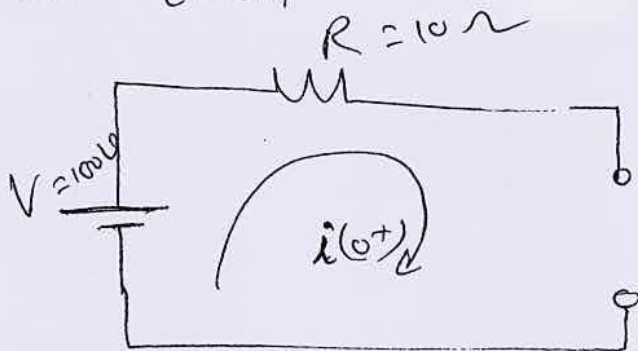

eqt ckt at $t=0+$
is of known.

$$\therefore \boxed{i(0+) = 0}$$

for ① ~~at $t=0$~~
~~differentiating~~ $0 = R \frac{di}{dt}$

$$L \frac{di}{dt} = V - Ri \quad \text{--- (2)} \quad \therefore \frac{di}{dt} = \frac{V - Ri}{L}$$

$$\text{at } t=0+ \quad \frac{di(0+)}{dt} = \frac{V - Ri(0+)}{L}$$

$$\frac{di}{dt}(0+) = \frac{100 - 10(0)}{1} = \boxed{100 \text{ A/sec}}$$

Diff ② $L \frac{d^2i}{dt^2} = -R \frac{di}{dt}$

at $t=0+$

$$\frac{d^2i(0+)}{dt^2} = -\frac{R}{L} \frac{di(0+)}{dt}$$

11/8 Aug 2004 (10M)
Jan 2009 11/8 prob.


June 2010 (10M)

$$\boxed{\frac{d^2i}{dt^2}(0+) = -\frac{10}{1} 100 = -1000 \text{ A/sec}^2}$$

④ In the network shown in fig. K is changed from position a to b at $t=0$. Solve for 'i'.

$\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0+$, if $R=100\Omega$, $L=1\text{H}$, $C=0.1$

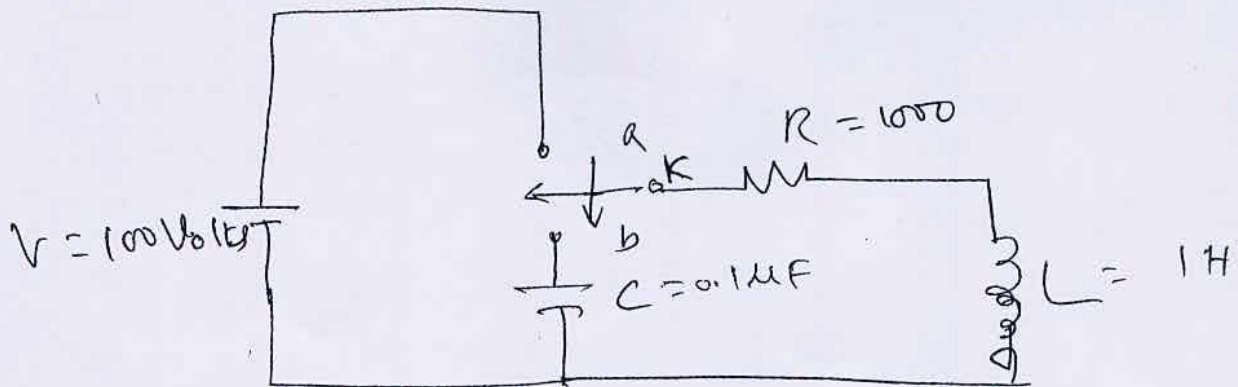and $V=100\text{V}$. Assume that the capacitor is initially uncharged.



When the switch is at 'a' inductor acts as a short ckt (network is under steady state)

$$i(0^-) = \frac{V}{R} = \frac{100}{1000} = \boxed{0.1 \text{ A}}$$

$$\therefore i(0^+) = 0.1 \text{ A}$$

i.e. the inductor has an initial current of 0.1 A

When K is changed from a to b, $i(0^+) = 0.1 \text{ A}$

When K is at 'b'

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad \text{--- (3)}$$

$$\text{at } t=0^+, \quad R i(0^+) + L \frac{d i(0^+)}{dt} + \frac{1}{C} \int i(0^+) dt = 0.$$

It is given that $\frac{1}{C} \int i(0^+) dt = V_C @ t=0^+ = 0$. (Capacit is initially uncharged)

$$L \frac{d i}{dt} (0^+) = -R i(0^+)$$

$$\frac{d i}{dt} (0^+) = -\frac{R}{L} i(0^+) = -\frac{1000}{1} (0.1) = -100 \text{ A/s}$$

Diff (3)

$$R \frac{d i}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C} = 0$$

at $t=0^+$

$$R \frac{d i}{dt} (0^+) + L \frac{d^2 i}{dt^2} (0^+) + \frac{i(0^+)}{C} = 0$$


$$R. 1000 (-100) + L \frac{d^2 i}{dt^2} (0^+) + \frac{0.1}{0.1 \times 10^{-6}} = 0$$

at

$$L \frac{d^2 i}{dt^2} = -10^6 + 10^5 = -9 \times 10^5$$

$$\therefore \frac{d^2 i}{dt^2} = \frac{-9 \times 10^5}{1} = -9 \times 10^5 \text{ A/s}^2$$

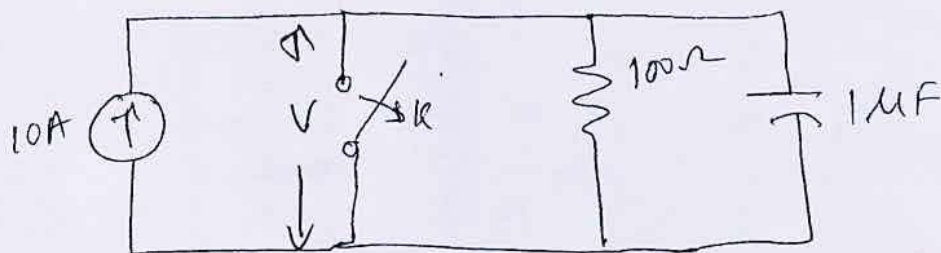⑤ In the circuit shown in the figure the switch 'K' is opened at $t=0$, find the values of V , $\frac{dV}{dt}$ at $t=0^+$



When the switch 'K' is closed all the current flows through the S.C. The capacitor is not charged as it acts as an O.C. $V_C(0^-) = 0 = V_C(0^+)$

When 'K' is opened,

$$-10 + \frac{V}{100} + C \frac{dV}{dt} = 0 \quad \therefore \frac{V}{100} + C \frac{dV}{dt} = 10$$

$$C \frac{dV}{dt} = 10 - \frac{V}{100}$$

$$\therefore \frac{dV}{dt} = \frac{10}{C} - \frac{V}{100C} \quad \text{--- (1)}$$

at $t=0^+$

$$\frac{dV}{dt}(0^+) = \frac{10}{10^{-6}} - \frac{V(0^+)}{100 \times 10^{-6}}$$

$$\boxed{\frac{dV}{dt}(0^+) = 10^7 \text{ V/sec}}$$

Diff (1) wr to 't'

$$\frac{d^2V}{dt^2} = 0 - \frac{1}{100C}$$

$$\frac{d^2V}{dt^2} = -\frac{1}{100C} \frac{dV}{dt}$$


at $t=0^+$

$$\begin{aligned} \frac{d^2V}{dt^2}(0^+) &= -\frac{1}{100 \times 10^{-6}} \times 10^7 \\ &= -\frac{1}{100 \times 10^{-6}} \times 10^7 = -10 \text{ V/sec}^2 \end{aligned}$$

⑥ In the network shown in fig 'K' is changed from the position it takes at $t=0$. Solve for 'K'.

~~July~~ May/June 2010 (10M)

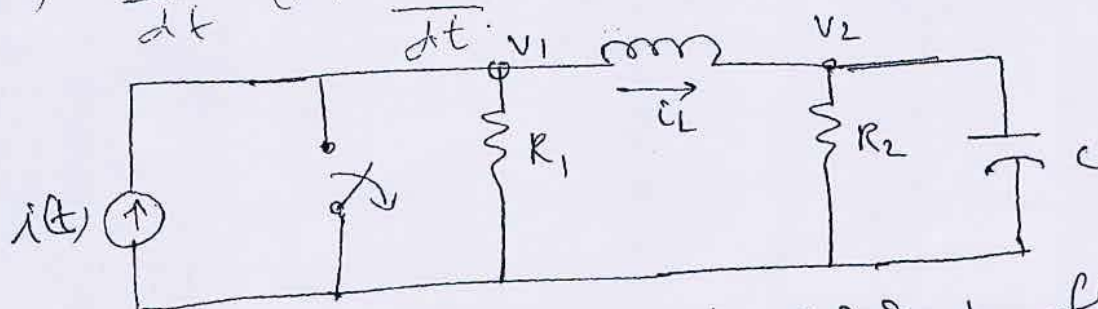⑥ In the network shown in fig. 'K' changes from $\downarrow$ to $\uparrow$ has two independent node pairs. If the switcher 'K' is opened at $t=0$, find the following quantities at $t=0^+$, (i) V_1 (ii) V_2 (iii) $\frac{dV_1}{dt}$ (iv) $\frac{dV_2}{dt}$ (v) $\frac{dI_L}{dt}$



When the 'K' is closed, all the current flows through S.C. & hence $I_L(0^-) = 0$, $V_C(0^-) = 0$

$$\therefore I_L(0^+) = 0, \therefore V_C(0^+) = 0$$

$$\therefore \boxed{V_2(0^+) = 0}$$

When K is opened at $t=0$.

$$\text{For node } V_1, \quad i(t) = \frac{V_1}{R_1} + I_L \quad \text{--- (1)}$$

$$\text{at } t=0^+, \quad I(0^+) = \frac{V_1(0^+)}{R_1} + 0 \quad \therefore \boxed{V_1(0^+) = I(0^+)R_1}$$

$$\text{For Node (2),} \quad -I_L + \frac{V_2}{R_2} + C \frac{dV_2}{dt} = 0$$

$$\text{at } t=0^+, \quad -I_L(0^+) + \frac{V_2(0^+)}{R_2} + C \frac{dV_2(0^+)}{dt} = 0$$

$$0 + 0 + C \frac{dV_2(0^+)}{dt} = 0$$

$$\therefore \boxed{\frac{dV_2(0^+)}{dt} = 0}$$

Diff. eqn ① $\frac{di}{dt} = \frac{1}{R_1} \frac{dV_1}{dt} + \frac{di_L}{dt}$

$$\frac{di}{dt}(0+) = \frac{1}{R_1} \frac{dV_1(0+)}{dt} + \frac{di_L(0+)}{dt}$$

$$\frac{1}{R_1} \frac{dV_1(0+)}{dt} = \frac{di}{dt}(0+) - \frac{di_L(0+)}{dt} \quad \text{--- ②}$$

$$\frac{1}{R_1} \frac{dV_1(0+)}{dt} = \text{But } i_L = \frac{1}{L} \int (V_1 - V_2) dt$$

Diff $\frac{di_L}{dt} = \frac{1}{L} (V_1 - V_2)$

at $t=0+$

$$\frac{di_L(0+)}{dt} = \frac{1}{L} [V_1(0+) - V_2(0+)]$$

Sub in ②


$$\frac{di_L}{dt}(0+) = \frac{1}{L} [i(0+) R_1 - 0]$$

$$\therefore \frac{1}{R_1} \frac{dV_1(0+)}{dt} = \frac{di}{dt}(0+) - \frac{1}{L} [i(0+) R_1]$$

$$\therefore \frac{dV_1(0+)}{dt} = R_1 \left[\frac{di}{dt}(0+) + \frac{1}{L} R_1 i(0+) \right]$$

⑦ July 2009 | Jan 2007 (10M)

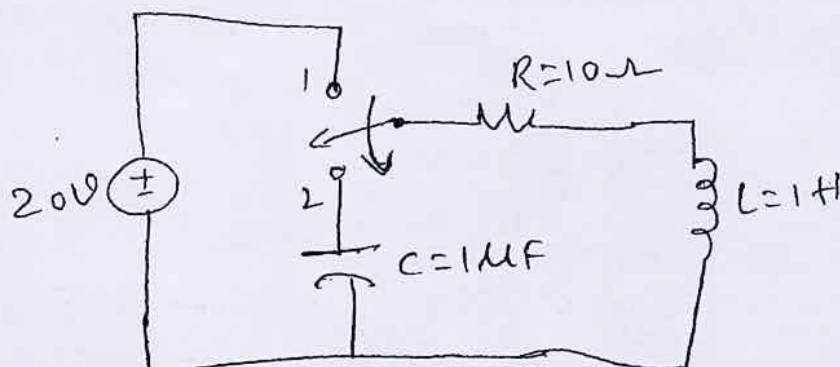For the circuit shown in fig, the switch 'K' is ~~initially~~ changed from position (1) to position (2) at $t=0$, (steady state condition having been reached in position (1)). Find the values of i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0$.



When the switch is at ①, the ckt is under steady state conditions, L acts as a s.c. & C acts as o.c.

$$i(0^-) = \frac{V}{R} = \frac{100}{10} = 10 \text{ A} = i(0^+)$$

$$V_C(0^-) = 0 = V_C(0^+)$$

When the switch is changed from ① to ②

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad \text{--- ①}$$

at $t=0^+$

$$Ri(0^+) + L \frac{di}{dt}(0^+) + \frac{1}{C} \int i(0^+) dt = 0$$

$$(10)(10) + 1 \frac{di}{dt}(0^+) + V_C(0^+) = 0$$

$$\boxed{\frac{di}{dt}(0^+) = -1000 \text{ A/sec}}$$

Diff ①

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0$$

at $t=0^+$


$$R \frac{di}{dt}(0^+) + L \frac{d^2i}{dt^2}(0^+) + \frac{i(0^+)}{C} = 0$$

$$10(-1000) + 1 \cdot \frac{d^2i}{dt^2}(0^+) + \frac{10}{10^{-6}} = 0$$

$$\boxed{\frac{d^2i}{dt^2}(0^+) = 10^7 + 10^4 = 10^4(1010) \text{ A/sec}^2} \quad \text{verify}$$

June 2012

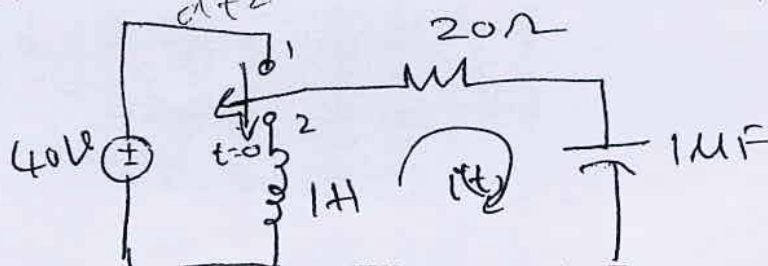Q3) Jan 2009 For the network shown in fig, the switch is moved from position 1 to position 2 at $t=0$, steady state has been reached before switching. Calculate i , $\frac{di}{dt}$, $\frac{d^2i}{dt^2}$ at $t=0$



When the switch is on, 'L' acts as S.C. & C acts as O.C. as the circuit is under steady state condn. at $t=0^-$, $\boxed{i(0^-) = \frac{20}{10} = 2A = i(0^+)}$

When 'K' is changed from (1) to (2), $V_C(0^-) = 0 = V_C(0^+)$

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int i dt = 0 \quad \text{--- (1)}$$

at $t=0^+$

$$Ri(0^+) + L \frac{di(0^+)}{dt} + \underbrace{\frac{1}{C} \int i(0^+) dt}_{V_C(0^+) = 0} = 0$$

$$\therefore L \frac{di}{dt}(0^+) = -R i(0^+) = -(10)(2) = -20A$$

$$\therefore \boxed{\frac{di}{dt}(0^+) = \frac{-20}{L} = \frac{-20}{1} = -20A/sec.}$$

Diff (1)

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i = 0$$

$$L \frac{d^2 i}{dt^2} = -\frac{i}{C} - R \frac{di}{dt}$$

at $t=0^+$

$$L \frac{d^2 i(0^+)}{dt^2} = -\frac{i(0^+)}{C} - R \frac{di(0^+)}{dt}$$

$$\frac{d^2 i(0^+)}{dt^2} = -\frac{i(0^+)}{LC} - \frac{R}{L} \frac{di(0^+)}{dt}$$

$$= -\frac{2}{(1)(1 \times 10^{-6})} - \frac{10}{1}(-20)$$

$$= -2 \times 10^6 + 200$$

$$= -2000000 + 200$$

$$\boxed{\frac{d^2 i(0^+)}{dt^2} = -19,998,000 A/s^2}$$


9) For the network shown in find out $i(t)$, $\frac{di}{dt}(0^+)$

$4 \frac{d^2 i}{dt^2}(0^+)$

July 2008 (7M)

Jan/Feb 2004 (6M)

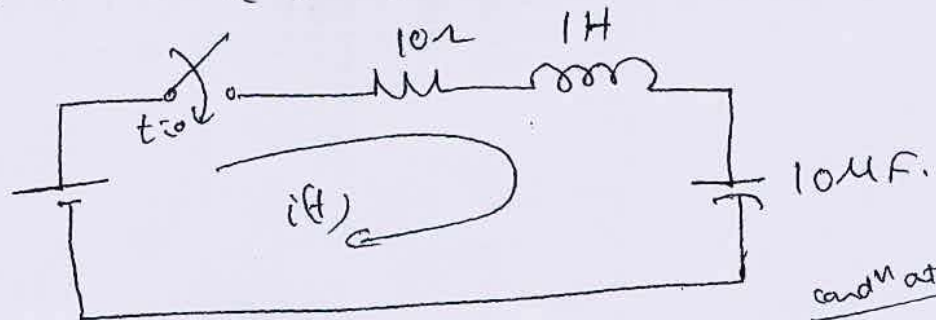take $V_c(0) = 0$, if K is closed at $t=0$



and at $t=0^+$

When 'K' is closed at $t=0$, L acts as 'o.c' & C acts as short circuit. $\therefore t=0^+$, $i(0^+) = 0$ & $V_c(0^+) = 0$

When switch closed at $t=0$, the general eqn for the circuit is
at $t=0^+$

$$R i(t) + L \frac{di}{dt} + \frac{1}{C} \int i dt = 10 \quad \text{--- (1)}$$

$$R i(0^+) + L \frac{di}{dt}(0^+) + \frac{1}{C} \int i(0^+) dt = 10$$

$$\therefore \frac{di}{dt}(0^+) = \frac{10}{L} = \frac{10}{1} = 10 \text{ A/sec} \quad V_c(0^+) = 0$$

Diff (1)

at $t=0^+$

$$R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i(t) = 0$$

$$L \frac{d^2 i}{dt^2}(0^+) = -\frac{1}{C} i(0^+) - R \frac{di}{dt}(0^+)$$

Jan 2006 (6M)


$$\frac{d^2 i(0^+)}{dt^2} = -\frac{10}{1} \cdot 10 = -100 \text{ A/sec}^2$$

10) A parallel R-L circuit is energized by a current source of 1A. The switch across the source is opened at $t=0$. Solve for V , DV , D^2V all $t=0^+$, if $R = 100\Omega$ & $L = 1H$.

$$V(0^+)$$

$$DV(0^+)$$

$$D^2V(0^+)$$

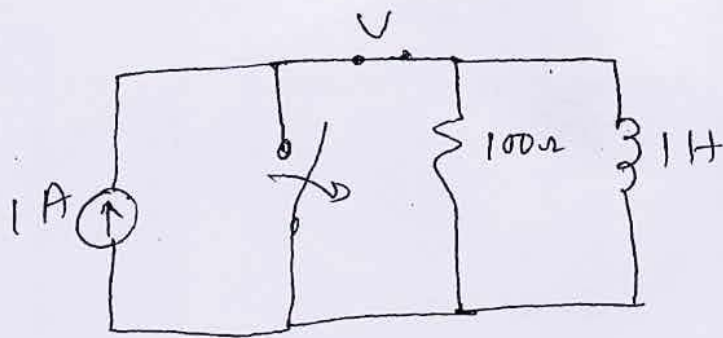

When the switch (12) is closed, all the current flows through short circuit.

Hence $i_L(0^-) = 0$, $V(0^-) = 0$

When switch is opened at $t = 0$, L acts as an o.c. all the current flows through resistor
($t = 0^+$ and on)

$$\therefore V(0^+) = 100 = 100 \text{ Volts}$$

The general eqn at $t = 0$ is given by

$$i(t) = \frac{V}{L} + \frac{1}{L} \int V dt \quad \text{--- (1)}$$

at $t = 0^+$ $i(0^+) = \frac{V(0^+)}{L} + \frac{1}{L} \int V(0^+) dt$

diff. $\frac{di(0^+)}{dt} = 0$ $0 = \frac{1}{L} \frac{dV(0^+)}{dt} + \frac{1}{L} V(0^+)$ --- (2)

diff (1) at $t = 0^+$ $\frac{1}{L} \frac{dV(0^+)}{dt} = -\frac{1}{L} V(0^+)$

$$\therefore \frac{dV(0^+)}{dt} = -\frac{100}{1} \times 100 = -10,000 \text{ V/sec.}$$

Diff (2).

$$\frac{1}{L} \frac{d^2 V(t)}{dt^2} + \frac{1}{L} \frac{dV(t)}{dt} = 0$$

$$\frac{1}{L} \frac{d^2 V(t)}{dt^2} = -\frac{1}{L} \frac{dV(t)}{dt}$$

at $t = 0^+$


$$\frac{d^2 V(0^+)}{dt^2} = -\frac{100}{1} \frac{dV(0^+)}{dt}$$

$$= -100 (-10,000)$$

$$\boxed{\frac{d^2 V(0^+)}{dt^2} = 10^6 \text{ V/Sec}^2}$$

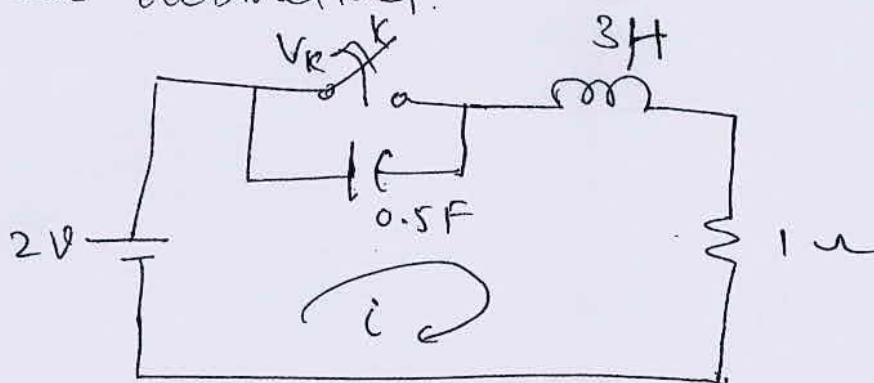(11) Jan/Feb 2005 (TOM) Jan 2015

$R=1\Omega$, $L=1H$, & $C=\frac{1}{2}F$ are in series with a switch across it. 2Volt is applied to circuit. At $t=0^-$, the switch is in closed. At $t=0$ the switch is opened. Find at $t=0^+$, the Voltage across the switch, its first and second order derivatives.



at $t=0^-$ There is a short circuit across capacitor.
 $\therefore V_C(0^-) = 0 = V_C(0^+)$

Under steady state condition Inductance acts as short circuit.

$$\therefore i(0^-) = \frac{2}{1} = \underline{2A} = i(0^+)$$

When the switch is opened $V_K = V_C$

$$\text{i.e. } V_K(0^-) = \boxed{V_K(0^+) = 0}$$

$$V_C = \frac{1}{C} \int i dt = V_K \quad \text{--- (1)}$$

Diff.

$$\frac{dV_K}{dt} = \frac{i}{C} \quad \text{--- (2)} \quad \therefore \text{at } t=0^+$$

$$\frac{dV_K}{dt}(0^+) = \frac{1}{C} i(0^+)$$

$$\therefore \boxed{\frac{dV_K}{dt}(0^+) = \frac{2}{0.5} = 4 \text{ V/sec}}$$

gen. eqn is

$$v = \frac{1}{C} \int i dt + L \frac{di}{dt} + Ri$$

at $t=0^+$

$$2 = \underbrace{\frac{1}{C} \int i(t) dt}_{V_K(t)} + L \frac{di}{dt}(t) + Ri(t)$$

$$2 = 0 + 3 \cdot \frac{di}{dt}(0^+) + 1(2) \quad \therefore \boxed{\frac{di}{dt}(0^+) = 0}$$

Diff² $\frac{d^2 V_K}{dt^2} = \frac{1}{C} \frac{di}{dt}$


at $t=0^+$ $\therefore \frac{dV_K}{dt}(0^+) = \frac{1}{C} i(0^+) = \frac{1}{0.5} = 2$

at $t=0^+$ $\frac{d^2 V_K}{dt^2}(0^+) = \frac{1}{C} \frac{di}{dt}(0^+) = \frac{1}{0.5} \cdot 0 = 0$

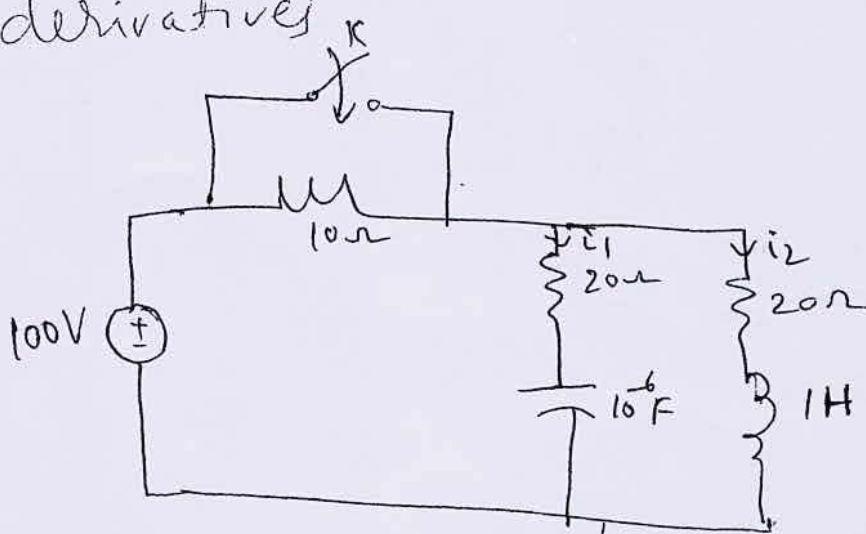(12) Jan/Feb 2006

(8M)

A series RLC circuit with $R = 20\Omega$ and $C = 1\mu F$ is shunted by an inductor of reactance 20Ω and inductance $1H$. This is supplied by a D.C. source of $100V$ through a series resistance of 10Ω . There is a switch across 10Ω which is closed at $t=0$. Solve for the currents in L & C and their first derivatives.



When 'K' is open, ckt is under steady state cond. Inductor acts as short ckt & Capacitor acts as open ckt.

$$\therefore i_L(0^-) = \frac{100}{20+10} = \frac{100}{30} A = i_L(0^+) = \frac{10}{3} A = i_C(0^+)$$

$$i_C(0^-) = 0, \therefore i_C(0^-) = i_C(0^+)$$

$$V_C(0^-) = 100 - (10)\left(\frac{10}{3}\right) = \frac{200}{3} \text{ V} \stackrel{!}{=} V_C(0^+) \quad (15)$$

When 'K' is closed at $t=0$, the general equations are

$$100 = 20i_1 + \frac{1}{10^{-6}} \int i_1 dt$$

at $t=0^+$

$$100 = 20i_1(0^+) + V_C(0^+)$$

$$\therefore i_1(0^+) = \frac{100 - \frac{200}{3}}{20} = \frac{\frac{100}{3}}{20} = \frac{10}{6} \text{ A}$$

$$20i_1 + 10^6 \int i_1 dt = 100 \quad (1)$$

$$\frac{di_2}{dt} + 20i_2 = 100 - V_C(0^+) \quad (2)$$

$$i_1(0^+) = \frac{100 - 10^6 \int i_1 dt}{20} = \frac{100 - \frac{200}{3}}{20} = \frac{\frac{100}{3}}{20} = \frac{5}{6} \text{ A}$$

$$i_1(0^+) = \frac{5}{6} \text{ A} \quad \text{and} \quad i_2(0^+) = \frac{10}{6} \text{ A} \quad (\text{known from (1)})$$

$$\text{Diff (1)} \quad 20 \frac{di_1}{dt} + 10^6 i_1 = 0$$

$$\text{at } t=0^+ \quad \frac{di_1}{dt} = \frac{-10^6 i_1(0^+)}{20} = \frac{-10^6 \cdot \frac{5}{6}}{20} = -\frac{5 \times 10^5}{6} \text{ A/sec.}$$

$$\boxed{\frac{di_1}{dt}(0^+) = -83,333 \text{ A/sec}}$$


at $t=0^+$

$$\frac{di_2}{dt}(0^+) = 100 - 20i_2(0^+) = 100 - 20\left(\frac{10}{6}\right)$$


$$\boxed{\frac{di_2}{dt}(0^+) = 33.33 \text{ A/sec}}$$

~~July 2006~~ July 2006 (10M)

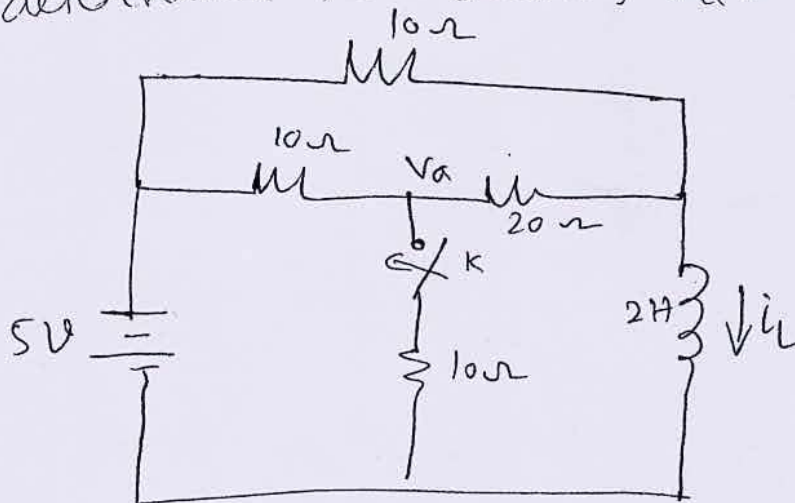- (13) In the network shown in fig steady state is reached with the switch K open. At $t=0$, the switch is closed. For the element values give determine the values $V_a(0^-)$ & $V_a(0^+)$



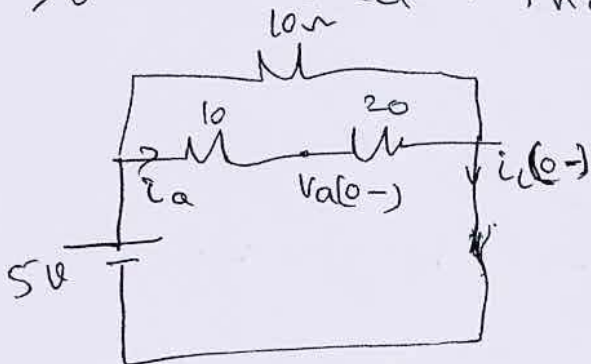When switch is open ckt is at steady state and inductor acts as short ckt



$$i_L(0^-) = \frac{5}{10 + 20} = \frac{5}{30} = \frac{1}{6} \text{ A}$$

$$= \frac{1 + 3}{6} = \frac{4}{6} = \frac{2}{3}$$

$$i_L(0^-) = 0.671$$

$$V_a(0^-) = 0.671 \times 20 = 13.42 \text{ V}$$

$$i_a = \frac{0.671 \times 10}{30} = 0.2235 \text{ A}$$


$$V_a(0^-) = 0.2235 \times 20 = 4.47 \text{ V}$$

$$i_L(0^-) = \frac{5}{10 + 20} = \frac{5}{30} = 0.167 \text{ A} = i_L(0^+)$$

$$i_a(0^-) = \frac{0.167 \times 10}{30} = 0.0557 \text{ A}$$

$$\therefore V_a(0^-) = i_a(0^-) \times 20 = 0.0557 \times 20 = 1.114 \text{ V}$$

When the switch K is closed at $t=0$

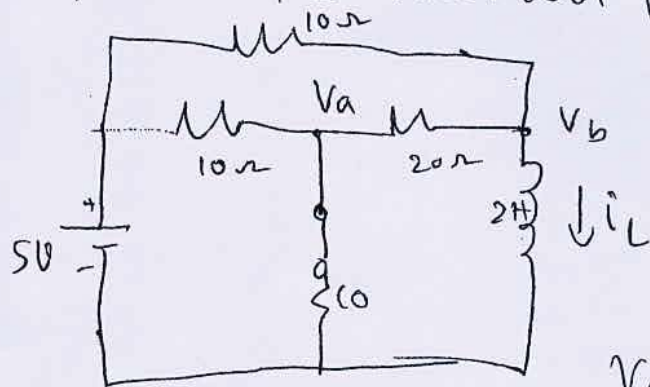

For node 'a' at $t=0^+$

$$\frac{V_a(t) - 5}{10} + \frac{V_a}{10} + \frac{V_a(t) - V_b}{20} = 0$$

$$V_a(t) \left[\frac{1}{10} + \frac{1}{10} + \frac{1}{20} \right] - \frac{V_b}{20} = \frac{5}{10}$$

$\times 4 \text{ by } 20$

$$V_a(t) [2 + 2 + 1] - V_b(t) = 10$$

For Node (b)

$$5V_a(t) - V_b(t) = 10 \quad \text{--- (1)}$$

$$\frac{V_b(t) - V_a(t)}{20} + \frac{V_b - 5}{10} + i_L(t) = 0$$

$$V_b(t) \left[\frac{1}{20} + \frac{1}{10} \right] - \frac{V_a(t)}{20} = -i_L(t) + \frac{5}{10}$$

$\times 4 \text{ by } 20$

$$- \frac{1}{20} V_a(t) + \left[\frac{1}{20} + \frac{1}{10} \right] V_b(t) = -i_L(t) + \frac{5}{10}$$


$$-V_a(t) + [1 + 2] V_b(t) = -20 i_L(t) + 10$$


$$-V_a(t) + 3V_b(t) = -20(-0.67) + 10 = -3.4$$

$$\boxed{V_a(t) = 1.9 \text{ volts}}$$

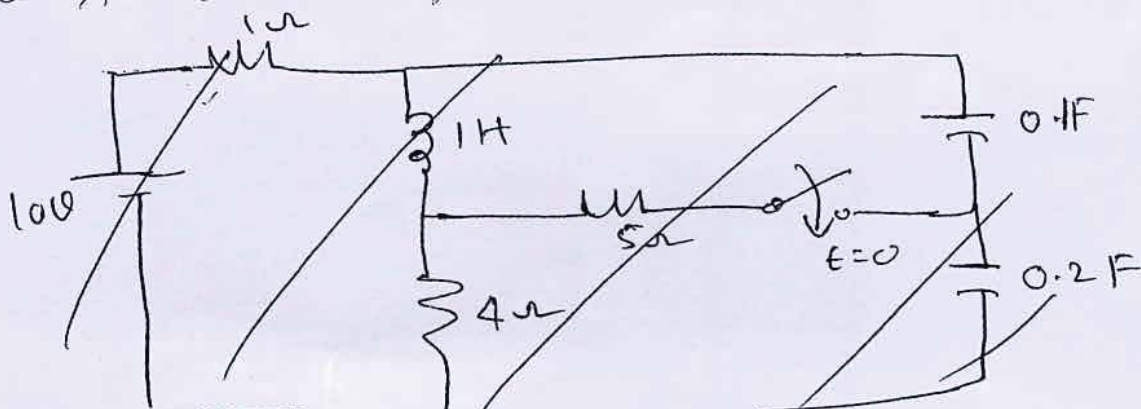
114) Jan 2008 For the network shown in fig, find $i_1, i_2, \frac{di_1}{dt}, \frac{di_2}{dt}, \frac{d^2i_2}{dt^2}$ at $t=0^+$

Circuit was in steady state before the closure of the switch. Assume all initial conditions are zero.



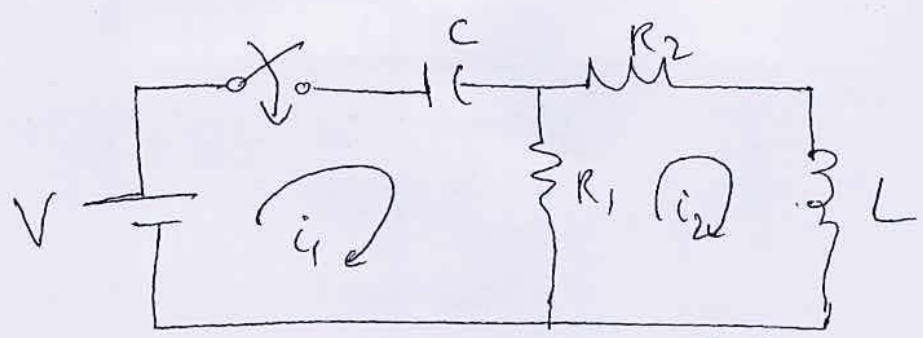

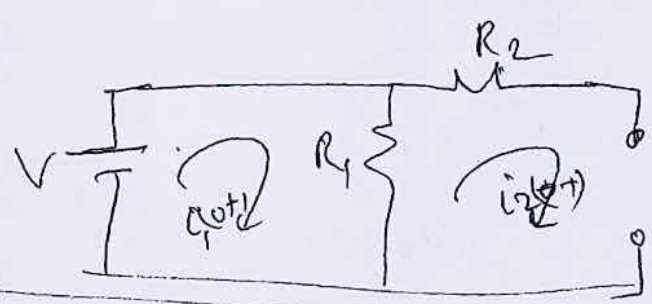
Network at $t = 0^+$, is as shown in fig.



$$i_1(0^+) = \frac{V}{R_1}, \quad i_2(0^+) = 0$$

writing loop equations for loop 1 & 2

~~$R_1 i_1 + V = 0$~~

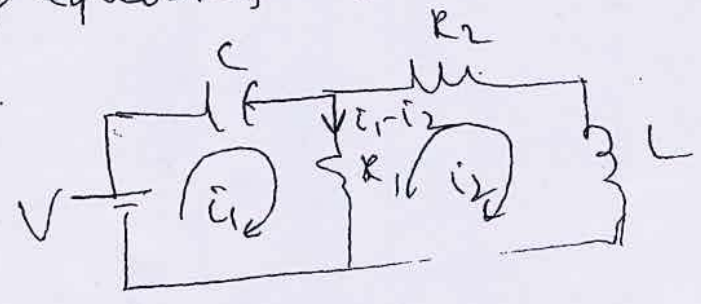

$$V = \frac{1}{C} \int \dot{i}_1 dt + R_1(i_1 - i_2) \quad \text{--- ①}$$

$$-R_2 i_2 + L \frac{di_2}{dt} + R_1(i_1 - i_2) = 0 \quad \text{--- ②}$$

Substituting I.C. in eqn ②

$$R_2 i_2(0^+) + L \frac{di_2}{dt}(0^+) - R_1 [i_1(0^+) - i_2(0^+)]$$

$$0 + L \frac{di_2}{dt}(0^+) - R_1 \left[\frac{V}{R_1} \right]$$

$$\therefore \left[\frac{di_2}{dt}(0^+) = + \frac{R_1}{L} \right]$$

Diff eqn ①

at $t=0+$,

$$\frac{\dot{i}_1}{C} + R_1 \left(\frac{d\dot{i}_1}{dt} - \frac{d\dot{i}_2}{dt} \right) = 0 \quad (3)$$

$$\frac{\dot{i}_1(0+)}{C} + R_1 \frac{d\dot{i}_1(0+)}{dt} - R_1 \frac{d\dot{i}_2(0+)}{dt}$$

$$\therefore R_1 \frac{d\dot{i}_1(0+)}{dt} = R_1 \frac{d\dot{i}_2(0+)}{dt} - \frac{\dot{i}_1(0+)}{C}$$

$$= R_1 \frac{V}{L} - \frac{V}{R_1 C}$$

$$\therefore \boxed{\frac{d\dot{i}_1(0+)}{dt} = \frac{V}{L} - \frac{V}{R_1^2 C}}$$

Diff eqn ②

$$-R_2 \frac{d\dot{i}_2}{dt} - L \frac{d^2 \dot{i}_2}{dt^2} + R_1 \left[\frac{d\dot{i}_1}{dt} - \frac{d\dot{i}_2}{dt} \right] = 0$$

$$L \frac{d^2 \dot{i}_2}{dt^2} = R_2 \frac{d\dot{i}_2}{dt} + R_1 \left[\frac{d\dot{i}_1}{dt} - \frac{d\dot{i}_2}{dt} \right]$$

at $t=0+$

$$L \cdot \frac{d^2 \dot{i}_2}{dt^2} = R_2 \frac{d\dot{i}_2(0+)}{dt} + R_1 \frac{d\dot{i}_1(0+)}{dt} - R_1 \frac{d\dot{i}_2(0+)}{dt}$$

$$= R_2 \frac{V}{L} + R_1 \left[\frac{V}{L} - \frac{V}{R_1^2 C} \right] - R_1 \left[\frac{V}{L} \right]$$

$$L \frac{d^2 \dot{i}_2(0+)}{dt^2} = R_2 \frac{V}{L} - \frac{V}{R_1 C}$$

$$\boxed{\frac{d^2 \dot{i}_2(0+)}{dt^2} = \frac{R_2 V}{L^2} - \frac{V}{R_1 L C}}$$

Differentiating eqn ③

$$\frac{1}{C} \frac{d\dot{i}_1}{dt} + R_1 \left[\frac{d^2 \dot{i}_1}{dt^2} - \frac{d^2 \dot{i}_2}{dt^2} \right] = 0$$

$$R_1 \frac{d^2 \dot{i}_1}{dt^2} = R_1 \frac{d^2 \dot{i}_2}{dt^2} - \frac{1}{C} \frac{d\dot{i}_1}{dt}$$

at $t=0+$

$$\frac{d^2 i_1}{dt^2}(0+) = \frac{d^2 i_2}{dt^2}(0+) - \frac{1}{R_C} \frac{di_1}{dt}(0+)$$

$$= V \left[\frac{R_2}{L^2} - \frac{1}{R_1 L C} \right] - \frac{1}{R_C} \left[\frac{V}{L} - \frac{V}{R_1^2 C} \right]$$

$$= V \left[\frac{R_2}{L^2} - \frac{1}{R_1 L C} - \frac{1}{R_1 L C} + \frac{1}{R_1^3 C^2} \right]$$

$$\boxed{\frac{d^2 i_1}{dt^2}(0+) = V \left[\frac{R_2}{L^2} - \frac{2}{R_1 L C} + \frac{1}{R_1^3 C^2} \right]}$$

(2)